



ECE 2214

Digital Logic Design

L-24 Registers and counters with CAD tools

Fall 2022



Outline



- * Use of registers and counters with schematics in QUARTUS II
- * Registers and counters in VHDL code
- * Registers and counters module instantiation
- * Use of sequential statement to implement registers and counters
- * Application example



Summary of previous lecture

- * Synchronous counters with D flip-flops
 - Not the best choice
 - Needs Enable to controls external logic
 - More complex design

- * N-bit implementation is achieved

$$D_0 = Q_0 \oplus E_N$$

$$D_1 = Q_1 \oplus Q_0 E_N$$

$$D_2 = Q_2 \oplus Q_1 Q_0 E_N$$

$$D_3 = Q_3 \oplus Q_2 Q_1 Q_0 E_N$$


...

...

...

$$D_n = Q_n \oplus Q_{n-1} \cdot \dots \cdot Q_1 Q_0 E_N$$

 - * Parallel loads are achieved with muxes at the D inputs
 - Select from parallel load of Q_x




A counter with parallel-load capability.



Summary of previous lecture


* Synchronous reset of counters

 - All changes in the circuit are clock synchronized
- Any N-bit binary counter resets automatically after reaching the number $2^N - 1$
- Preset and reset of F-F can be used to set the counter at any counting sequence
- Designer should select unique features of the counting sequence desired and implement a logic to activate the load/reset pin



* Asynchronous reset of counters

 - Any change in the counting sequence is active immediately
- External logic is also used to reset sequence
- Last counting sequence is of short duration
- Designer should count one state more to achieve proper counting



* Valid for down or up counters



Summary of previous lecture

* Other types of counters

▪ BCD counters

- ▶ A binary-coded counter base 10
- ▶ Each digit count from 0-9
- ▶ Any excess from the least significant digit (LCD) is added to the next digit
- ▶ **Similar procedure applies to counter in any other radix**
 - ▶ **i.e. Radix 13: need 4 bits to count from 0-C (0000-1100)**
any excess the LCD is added to the next digit

▪ Ring counters

- ▶ Special type of counters that only one of the outputs is ON at a time
- ▶ Shift the output circularly along all outputs


▪ Johnson counters

- ▶ A modification to the ring counter
- ▶ Q complemented of the last bit is fed back to the first input
- ▶ Circuit outputs two patterns 4-bit counter as:
(1000, 1100, 1110, 1111) & (0111, 0011, 0001, 0000)



Registers and counters with schematics in Quartus II

 
- * Flip-flops, registers and counters can be accomplished in many different ways in QUARTUS II
- * Implementation depends on design requirements
- * QUARTUS provides default modules for flip-flops and counters
- * T, D and JK flip-flops are available with clear and preset
- * Located in the “primitive” library





Registers and counters with schematics in Quartus II

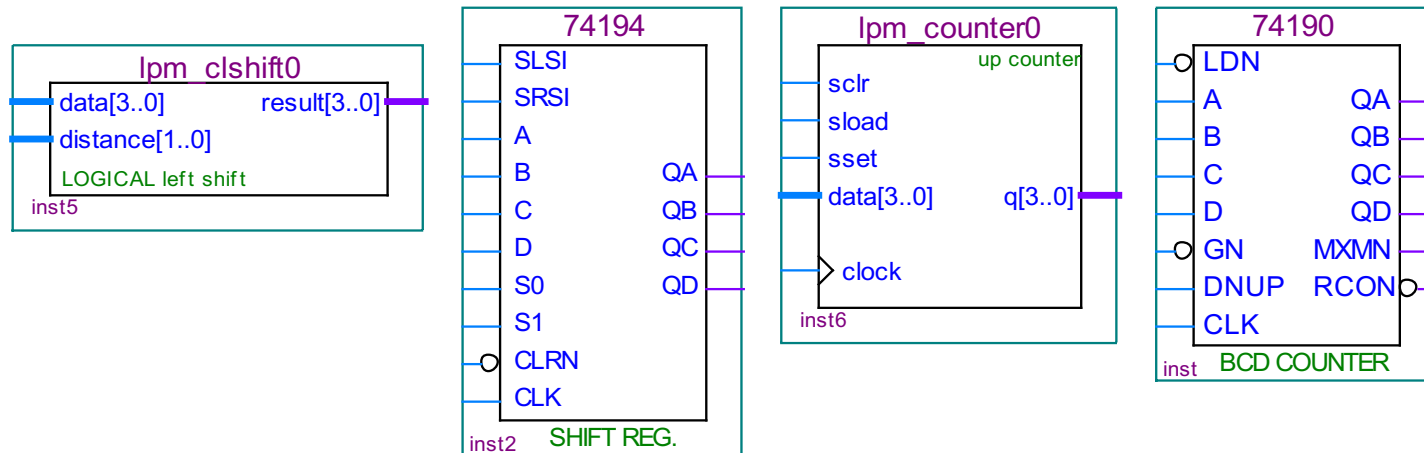- * Registers and counters have configurable pre-built modules



- * LPM (library of parameterized modules) also includes flip-flops, registers, counters and other useful circuits
 - Are configurable
- * Other libraries provide modules for commercially available circuits



Registers and counters in VHDL

- * Registers and counters are performed in several ways in QUARTUS II using VHDL
- * There are two main ways for the implementation:
 - Instantiate the pre-defined module from the LPM library
 - Implement the circuits with sequential statements
- * Register and counter module instantiation:
 - Open wizard from “\Tools\IP Catalog” in QUARTUS
 - Select a configurable pre-defined module that fit the design requirements
 - Declare the module as a component in your root level design
 - Use GENERIC MAP construction to assign values to the parameters of the instantiated sub-circuit
 - ▶ Similar to PORT MAP construction
 - Use PORT MAP construction to connect variables form the top-level design to the low-level design



Assigning constants and variables to a pre-built module in Quartus II

- * Values can be assigned when the component is instantiated as:

...

Instance: module_name

GENERIC MAP (Const_assign1,{ Const_assign_x})

PORT MAP (Var_assign1,{ Var_assign_x});

- * Note that values can be assigned to more than one variable
- * GENERIC MAP assigns **constant values** to variables defined in the pre-built module
- * PORT MAP assigns **external variables** to variables defined in pre-built module
- * Some variables are optional (will take the default values if not explicitly defined)
- * Careful revision of the module information is required in order to achieve the desired results



Example of pre-built module use in Quartus II



Example 1: Use of VHDL code to instantiate a LPM shift register module


```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
LIBRARY lpm ;
USE lpm.lpm_components.all ;
```

```
ENTITY shift IS
    PORT ( Clock      : IN    STD_LOGIC ;
          Reset       : IN    STD_LOGIC ;
          Shiftin, Load : IN    STD_LOGIC ;
          R           : IN    STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          Q           : OUT   STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
END shift ;
```

```
ARCHITECTURE Structure OF shift IS
BEGIN
```

```
    instance: lpm_shiftreg
        GENERIC MAP (LPM_WIDTH => 4, LPM_DIRECTION => "RIGHT")
        PORT MAP (data => R, clock => Clock, aclr => Reset,
            load => Load, shiftin => Shiftin, q => Q ) ;
```

```
END Structure ;
```

 



Example of pre-built module use in Quartus II



Example 2: Use of VHDL code to instantiate a LPM counter module


```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
LIBRARY lpm ;  
USE lpm.lpm_components.all ;
```

```
ENTITY Count4 IS  
    PORT ( Clock      : IN    STD_LOGIC ;  
          Load       : IN    STD_LOGIC ;  
          Reset      : IN    STD_LOGIC ;  
          R          : IN    STD_LOGIC_VECTOR(3 DOWNTO 0) ;  
          Q          : OUT   STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;  
END Count4 ;
```

```
ARCHITECTURE Behavior OF Count4 IS  
BEGIN
```

```
    Instance: lpm_counter  
        GENERIC MAP (LPM_WIDTH => 4, LPM_DIRECTION => "UP")  
        PORT MAP (data => R, clock => Clock, sclr => Reset,  
                 sload => Load, q => Q);
```

```
END Behavior;
```

 



Sequential statements to implement registers and counters

- * There are several forms to implement registers and counters
- * **Example 3.** Implementation of an N-bit register with asynchronous clear

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;
```

```
ENTITY regn IS
```

```
    GENERIC ( N : INTEGER := 16 ) ;
```

```
    PORT ( D          : IN    STD_LOGIC_VECTOR(N-1 DOWNTO 0) ;  
          Resetn, Clock : IN    STD_LOGIC ;  
          Q           : OUT   STD_LOGIC_VECTOR(N-1 DOWNTO 0) ) ;
```

```
END regn ;
```

```
ARCHITECTURE Behavior OF regn IS
```

```
BEGIN
```

```
    PROCESS ( Resetn, Clock )
```

```
    BEGIN
```

```
        IF Resetn = '0' THEN
```

```
            Q <= (OTHERS => '0') ;
```

```
        ELSIF Clock'EVENT AND Clock = '1' THEN
```

```
            Q <= D ;
```

```
        END IF ;
```

```
    END PROCESS ;
```

```
END Behavior ;
```

- * Code performs a register of any number of digits (variable N)
- * Assignment operator “:=” is used to set the default value of N
- * The GENERIC assignment (N=16) is equivalent to Q="0000000000000000"
- * The statement (OTHERS => '0') result in a '0' assigned to each bit regardless of the total number selected



Use of sequential statement to implement registers and counters

```
LIBRARY ieee ;
```

```
USE ieee.std_logic_1164.all ;
```

```
USE ieee.std_logic_unsigned.all ;
```

✱ **Example 4.** Implementation of a 4-bit up-counter

```
ENTITY upcount IS
```

```
    PORT ( Clock, Resetn, E : IN    STD_LOGIC ;
```

```
          Q                 : OUT STD_LOGIC_VECTOR (3 DOWNT0 0)) ;
```

```
END upcount ;
```

```
ARCHITECTURE Behavior OF upcount IS
```

```
    SIGNAL Count : STD_LOGIC_VECTOR (3 DOWNT0 0) ;
```

```
BEGIN
```

```
    PROCESS ( Clock, Resetn )
```

```
    BEGIN
```

```
        IF Resetn = '0' THEN
```

```
            Count <= "0000" ;
```

```
        ELSIF (Clock'EVENT AND Clock = '1') THEN
```

```
            IF E = '1' THEN
```

```
                Count <= Count + 1 ;
```

```
            ELSE
```

```
                Count <= Count ;
```

```
            END IF ;
```

```
        END IF ;
```

```
    END PROCESS ;
```

```
    Q <= Count ;
```

```
END Behavior ;
```

- ✱ External variables can not be assigned more than twice inside the sequential statement
 - Error produced due to assignment of multiple constants to a variable
- ✱ Required a local variable (Count)
- ✱ You can assign the local variable before or after the sequential assignment
- ✱ Compiler generates a multiplexer




Application example of counters

- ✧ Design of a circuit to measure the reaction time of a person
- ✧ **Motivation:**
 - Digital circuits function at a remarkable speed: average delay of logic gates can be in the order of few nanoseconds
 - Human's reaction is very slow compared to the speed of digital circuits
 - Let's construct a circuit that can measure the reaction time of a person for a specific event
 - The event is the time response of a person detecting a small light on (Light emitting diode, LED)
 - The reaction time is measured when the person press a switch and turn the light off
- ✧ **System description:**
 - 2-digit system to display up to a hundred fractions of a second
 - The clock available changes at a rate of 102.4kHz



Application example

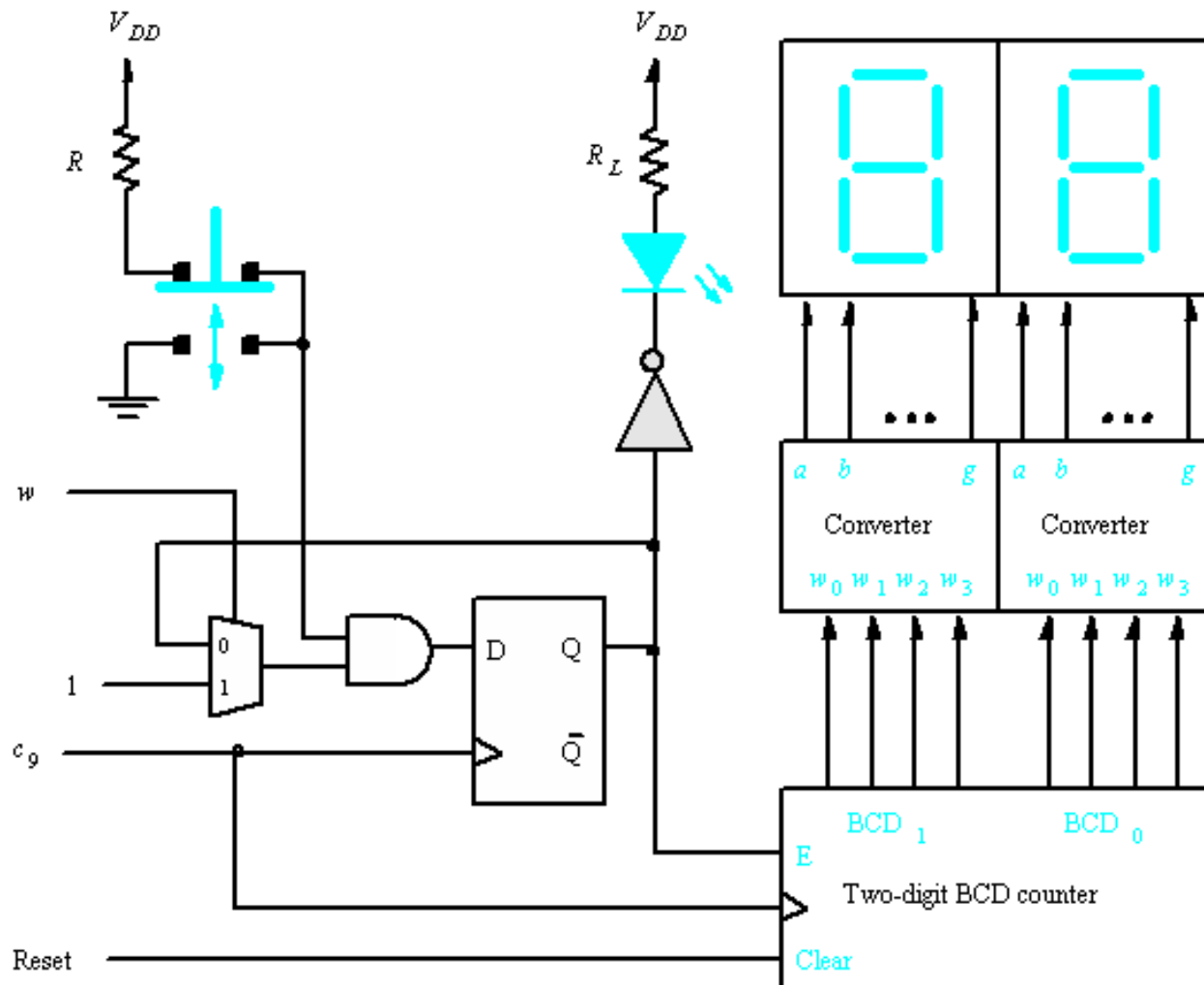



Application example


* Implementation:

- **Clock signal:** Usually of high frequency to control many synchronic processes in the design and also to ensure stability of the clock signal
- Clock should be reduced to 100Hz to measure the time at a resolution of 1/100 seconds (from 0/100 to 99/100)

* A binary counter can be used to divide the original clock signal and obtain the 100Hz signal needed. Calculation of the number of bit or flip-flops needed:

$$102400 \text{ Hz} / 100 \text{ Hz} = 1024$$

 - We know from previous lectures that binary counter divide numbers by 2^N , with N being the number of bits. Therefore $2^N = 1024$
 - Need a counter with 10 bits






Application example

* LED circuit:

 - The LED will emit light when current flows through the device
 - Current controlled by the NOT gate
- * If the output of the NOT gate is '0', V_{LED} is ON (a current flows to ground through the lower transistor)
- * If the output of the NOT gate is '1', V_{LED} is OFF (same potential is applied in both terminals of the LED).
- * Note that V_{LED} is controlled by the output Q of the D flip-flop






Application example



* Controlling the switch to reset the LED:


- LED has to be “ON” when the event “light” occurs
- LED should be “OFF” when switch is pressed
- The clock signal and the switch input have to be gated to stop the clock signal when the switch is pressed
- The input **w** is needed to start the reaction measurement
- $w = 1$ output a 1 from the multiplexer
- It is combined with the ‘1’ from the switch in default state
- This makes the output of the F-F to 1 and ...
- Switch the LED “ON”

 



Application example

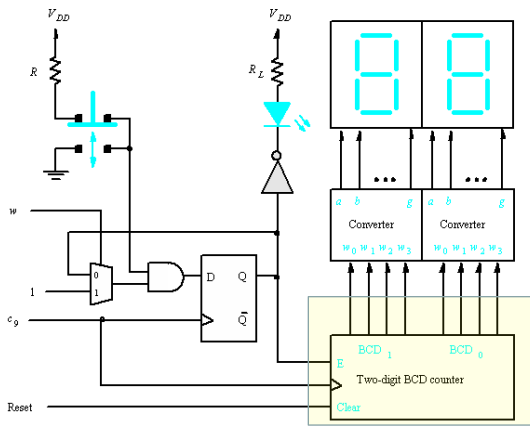- * **Counter:**
- * Counting the time signal
- * Display counting in BCD (0-99)/100 seconds
- * Two digit are needed
- * Clock provides the time base
- * Reset enable to re-start the measurement
- * Two-digit BCD counter can be implemented in VHDL as:



```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;

ENTITY BCDcount IS
    PORT (    Clock      : IN      STD_LOGIC ;
            Clear, E      : IN      STD_LOGIC ;
            BCD1, BCD0    : BUFFER  STD_LOGIC_VECTOR(3 DOWNTO 0) );
END BCDcount ;

ARCHITECTURE Behavior OF BCDcount IS
BEGIN
    PROCESS ( Clock )
    BEGIN
        IF Clock'EVENT AND Clock = '1' THEN
            IF Clear = '1' THEN
                BCD1 <= "0000" ; BCD0 <= "0000" ;
            ELSIF E = '1' THEN
                IF BCD0 = "1001" THEN
                    BCD0 <= "0000" ;
                    IF BCD1 = "1001" THEN
                        BCD1 <= "0000" ;
                    ELSE
                        BCD1 <= BCD1 + '1' ;
                    END IF ;
                ELSE
                    BCD0 <= BCD0 + '1' ;
                END IF ;
            END IF ;
        END IF ;
    END IF ;
END IF ;
```



Application example




* The whole reaction timer application can be implemented in VHDL

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY reaction IS
    PORT ( c9, Reset      : IN          STD_LOGIC ;
          w, Pushn       : IN          STD_LOGIC ;
          LEDn           : OUT         STD_LOGIC ;
          Digit1, Digit0 : BUFFER      STD_LOGIC_VECTOR(1 TO 7) ) ;
END reaction ;

ARCHITECTURE Behavior OF reaction IS
    COMPONENT BCDcount
        PORT ( Clock      : IN          STD_LOGIC ;
              Clear, E     : IN          STD_LOGIC ;
              BCD1, BCD0   : BUFFER      STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
    END COMPONENT ;
    COMPONENT seg7
        PORT ( bcd        : IN          STD_LOGIC_VECTOR(3 DOWNTO 0) ;
              leds         : OUT         STD_LOGIC_VECTOR(1 TO 7) ) ;
    END COMPONENT ;
    SIGNAL LED : STD_LOGIC ;
    SIGNAL BCD1, BCD0 : STD_LOGIC_VECTOR(3 DOWNTO 0) ;
```

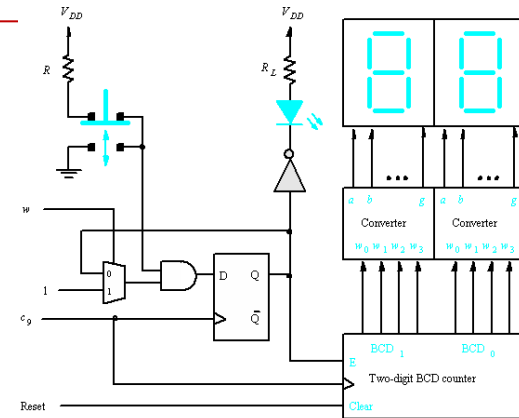




Application example

```
BEGIN
  flipflop: PROCESS (c9,Pushn,w)
  BEGIN
    WAIT UNTIL c9'EVENT AND c9 = '1' ;
    IF Pushn = '0' THEN
      LED <= '0' ;
    ELSIF w = '1' THEN
      LED <= '1' ;
    END IF ;
  END PROCESS ;

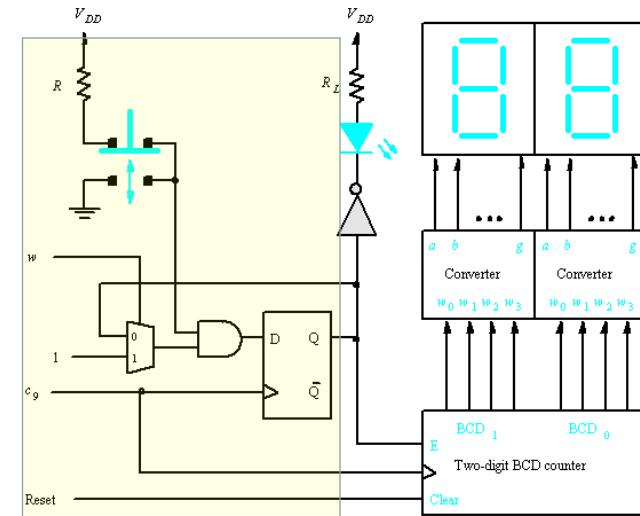  LEDn <= NOT LED ;
  counter: BCDcount PORT MAP ( c9, Reset, LED, BCD1, BCD0 ) ;
  seg1 : seg7 PORT MAP ( BCD1, Digit1 ) ;
  seg0 : seg7 PORT MAP ( BCD0, Digit0 ) ;
END Behavior ;
```



- * Notice that c9 is the output of bit 9 of the counter used to reduce the frequency of the original clock to 100Hz
- * It is not shown in this design



Summary

* Introduced

- Implementation of registers and counters in QUARTUS II using schematics
- Registers and counters in VHDL code
 - ▶ Register and counter module instantiation
 - ▶ Use of sequential statement to implement registers and counters
- Application examples

* Reference

- Fundamentals of Digital Logic with VHDL Design 3/e, Stephen Brown, Zvonko Vranesic; McGraw-Hill, 2009. Chapter 7, pp. 423-471
- Digital Design; Principles and Practices. Fourth Edition. John F. Wakerly, Prentice Hall, 2006. ISBN 0-13-186389-4. Chapter 7, pp. 710-758

* Next lecture

- Summary of topics to be evaluated in midterm 2 next Lecture